

## EMF and Internal Resistance

To know what EMF and internal resistance are

To know how to measure internal resistance

TO be able to sketch and interpret a V-I graph, labelling the gradient and y-intercept

### Energy in Circuits

In circuits there are two fundamental types of component: energy *givers* and energy *takers*.

### Electromotive Force (emf), $\epsilon$

Energy givers provide an electromotive force, they force electrons around the circuit which transfer energy.

The size of the emf can be calculate using:

$$\epsilon = \frac{E}{Q}$$

This is similar to the equation we use to find voltage/potential difference and means the energy given to each unit of charge. We can think of this as the energy given to each electron.

*The emf of a supply is the p.d. across its terminals when no current flows*

**EMF is measured in Joules per Coulomb,  $JC^{-1}$  or Volts, V**

Energy takers have a potential difference across them, transferring energy from the circuit to the component.

emf = energy giver

p.d. = energy taker

Energy is conserved in a circuit so energy in = energy out, or:

$$\boxed{\text{The total of the emfs} = \text{The total of the potential differences around the whole circuit}}$$

### Internal Resistance, $r$

The chemicals inside a cell offer a resistance to the flow of current, this is the internal resistance on the cell.

**Internal Resistance is measured in Ohms,  $\Omega$**

### Linking emf and $r$

If we look at the statement in the box above and apply it to the circuit below, we can reach an equation that links emf and  $r$ .

Total emfs = total potential differences

$$\epsilon = (\text{p.d. across } r) + (\text{p.d. across } R) \quad \{\text{Remember that } V=IR\}$$

$$\epsilon = (I \times r) + (I \times R)$$


$$\epsilon = Ir + IR$$

$$\boxed{\epsilon = I(r+R)}$$

*The terminal p.d. is the p.d. across the terminals of the cell when a current is flowing*



$$\epsilon = \text{internal p.d.} + \text{terminal p.d.}$$

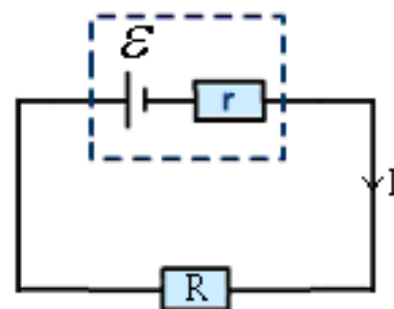So the above equation can be written as  $\epsilon = Ir + V$  where  $V$  is the terminal p.d.


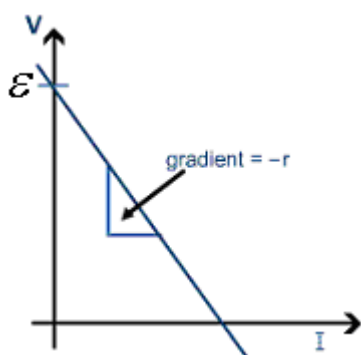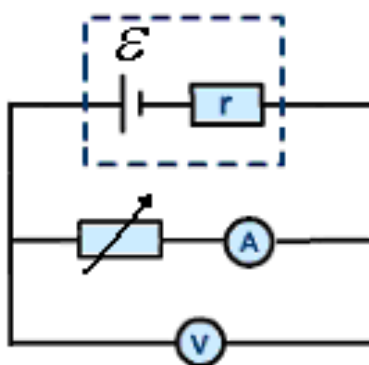
### Measuring emf and $r$

We can measure the emf and internal resistance of a cell by measuring the current and voltage as shown on the right, the variable resistor allows us to get a range of values. If we plot the results onto a graph of voltmeter reading against ammeter reading we get a graph that looks like the one below.



Graphs have the general equation of  $y = mx+c$ , where  $y$  is the vertical (upwards) axis,  $x$  is the horizontal (across) axis,  $m$  is the gradient of the line and  $c$  is where the line intercepts (cuts) the  $y$  axis.

If we take  $\epsilon = Ir + V$  and arrange it into  $y = mx + c$

