

## Kirchhoff's Laws and Potential Dividers

To know Kirchoff's Laws and be able to apply them to questions

To know what a potential divider is and be able to calculate the output voltage

To be able to explain an application of a potential divider

### **Kirchhoff's Laws**

Kirchhoff came up with two laws concerning conservation in electrical circuits.

#### **First Law**

Electric charge is conserved in all circuits, all the charge that arrives at a point must leave it.

Current going in = current going out.

In the diagram we can say that:

$$I_1 = I_2 + I_3 + I_4$$

#### **Second Law**


Energy is conserved in all circuits, for any complete circuit the sum of the emfs is equal to the sum of the potential differences.

Energy givers = energy takers.

In the diagram we can say that:

$$\epsilon = pd_1 + pd_2 + pd_3 + pd_4.$$

### **Potential Dividers**

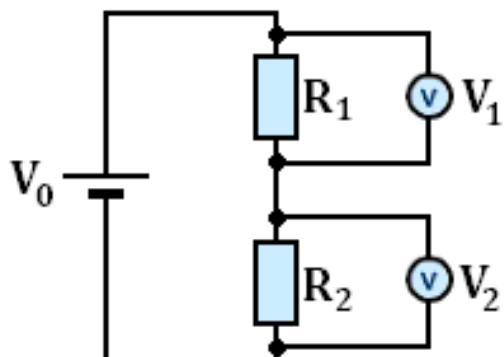

A potential divider is used to produce a desired potential difference, it can be thought of as a potential selector.

A typical potential divider consists of two or more resistors that share the emf from the battery/cell.

The p.d.s across  $R_1$  and  $R_2$  can be calculated using the following equations:

$$V_1 = V_0 \frac{R_1}{R_1 + R_2}$$

$$V_2 = V_0 \frac{R_2}{R_1 + R_2}$$

This actually shows us that the size of the potential difference is equal to the input potential multiplied by what proportion of  $R_1$  is of the total resistance.



If  $R_1$  is  $10\ \Omega$  and  $R_2$  is  $90\ \Omega$ ,  $R_1$  contributes a tenth of the total resistance so  $R_1$  has a tenth of the available potential. This can be represented using:

$$\frac{R_1}{R_2} = \frac{V_1}{V_2}$$


The ratio of the resistances is equal to the ratio of the output voltages.
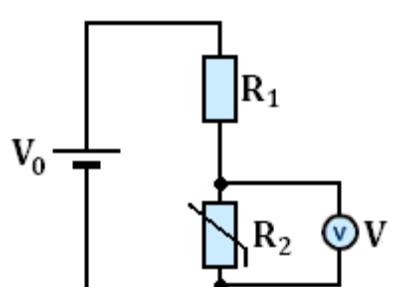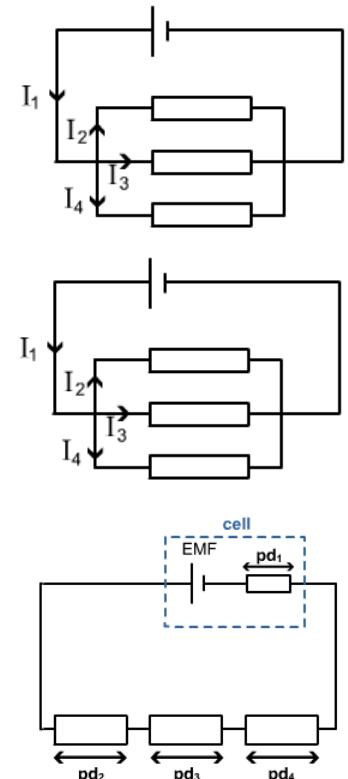
### **Uses**

In this potential divider the second resistor is a thermistor. When the temperature is low the resistance ( $R_2$ ) is high, this makes the output voltage high. When the temperature is high the resistance ( $R_2$ ) is low, this makes the



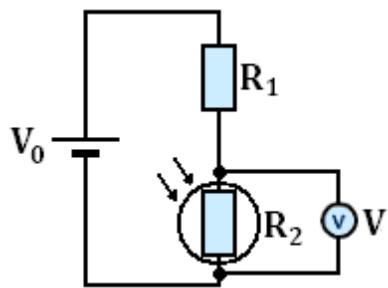output voltage low. A use of this would be a cooling fan that works harder when it is warm.



In the second potential divider the second resistor is a Light Dependant Resistor. When the light levels are low the resistance ( $R_2$ ) is high, making the output voltage high. When the light levels increase the resistance ( $R_2$ ) decreases, this makes the output voltage decrease. A use of this could be a street light sensor that lights up when the surrounding are dark.